

Work the following transistor problems from Fortney:

6-1

6-6 plus: suppose the temperature coefficient of V_{BE} is $2 \text{ mV}/^\circ\text{C}$, and the temperature changes from 20°C to 50°C . Calculate the new V_C for part (b).

6-8

6-9

6-10

6-17