

Lab #11 – Digital Circuits II

The purposes of this lab are

- to learn what a shift register is and how to construct one from flip-flops
- to learn what a counter is and how to use it to construct a divide-by-N circuit
- to become familiar with the 555-timer (one-shot) and to build an oscillator with it (only one of its many uses).


Equipment at each station:

digital oscilloscope
 2 multimeters, 2 power supplies
 signal generator, standard breadboard
 CMOS digital ICs: (4040 counter,
 4081 quad AND, 4013 dual flip-flop,
 555 monostable multivibrator)

Centrally available:

wire and wire cutters/stripper
 red and black banana plug cables
 assorted resistors and capacitors
 HP 3325 signal generator (up to 20 MHz)
 bags of LEDs

1. Shift Register from Flip-Flops

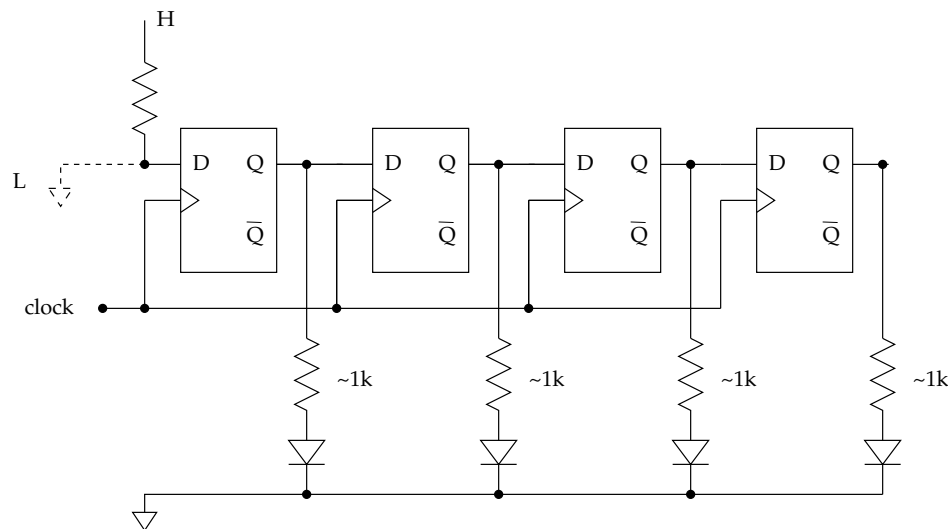

- Using two dual 4013 D flip-flops, build a 4-bit shift register as shown above. Include the LEDs and current limiting resistors on each output for visual confirmation of the *state* of your register. It may be necessary to increase the power supply voltage V_{DD} above 5V to drive the LEDs.
- Tie the input of your shift register to *high* through a “pull-up” resistor and attach a wire to the input so you can easily change the value of the input.
- Clock the shift register at some suitably low speed (~ 1 Hz) so that you can watch it in action. Apply a sequence of changing bits at the input and watch them move through the register.
- Optional: Connect all your shift registers together to make a giant register that can handle a larger *word*.
- Optional: Tie the output of the register to the input, making a circular register. How could you *load* this type of register?

2. Divide-by-N Counter

- Examine your 4040 12-bit ripple counter and its data sheet. Thankfully you can buy such a device and not have to build it from individual flip-flops! Connect V_{DD} to +5V and V_{SS} to ground. Connect a $5V_p$ square wave through an AC coupling capacitor. Unused inputs (e.g., reset) should be grounded.
- Verify that the outputs divide by 2^N . Monitor a few of them on your scope, or better yet, rig up some LEDs.
- Disconnect the *reset* and wave your hand around the IC. Note what happens and why unused CMOS inputs should be grounded.
- Using your scope, measure the delay for several different outputs, noting that the delay increases for progressively higher outputs. Increase the power supply voltage V_{DD} to 15V and note how the delay changes.
- Construct a “ $\div 5$ ” counter by feeding the appropriate outputs to an AND gate and into the reset.
- Optional: Connect our counter to your neighbors to make a 24-bit ripple counter.

3. Monostable Multivibrator



- Construct an oscillator for your counter using the 555 timer (a.k.a. “one-shot”). The figure above shows one way to make this circuit, including the pin numbers. An explanation of how this circuit works is given in the accompanying 555 data sheet.
- Examine the output before you put it into your counter.
- Optional: filter the output to remove the higher harmonics and produce something more like a sine wave.
- Optional: Use a trimpot to make the output frequency variable.