

Lab #9 – Operational Amplifiers II

The purposes of this lab are

- to construct an elementary differentiator or integrator circuit using an op-amp.
 - to construct at least one active filter (either low-pass, high-pass, band-pass, or notch), measure the transfer function, and cascade with other filters and observe the end-to-end transfer function.
 - to become familiar with the frequency counter.
-

Equipment at each station:


digital oscilloscope
 2 multimeters
 2 power supplies
 signal generator
 standard breadboard
 potentiometer
 frequency counter

Centrally available:

wire and wire cutters/stripper
 red and black banana plug cables
 alligator clips
 assorted resistors
 assorted capacitors
 op-amps (741 and 318)


1. Differentiator/Integrator

Differentiator:

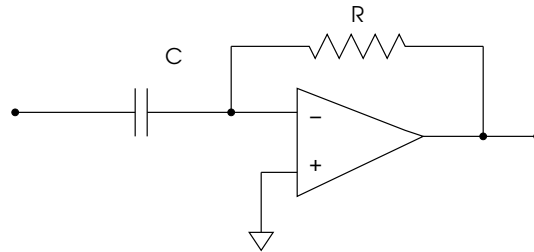

$R \sim 10k$
 $C \sim 2.2 \mu F$
 $f < 1 \text{ MHz}$

Integrator:




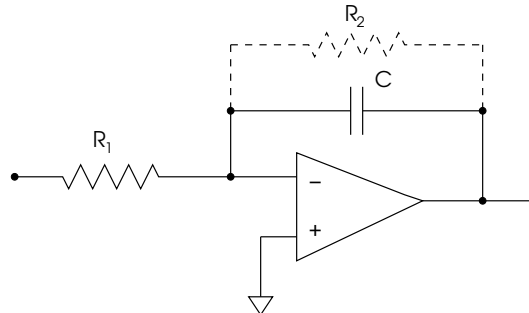


$R_1 \sim 10k$
 $R_2 \sim 10M$
 $C \sim 0.02 \mu F$
 $f \sim 1 \text{ kHz}$

- Construct an integrator or differentiator following the suggestions in the figures or in the book.
- Verify its functionality using a variety of input wave shapes.
- You might try different op-amps and different frequencies to determine when the circuit behaves non-ideally.
- Note: in the second circuit R_2 is needed to provide a DC feedback path. Without it, the DC gain is huge and amplifies even the tiny input voltage offset to nearly the rail.

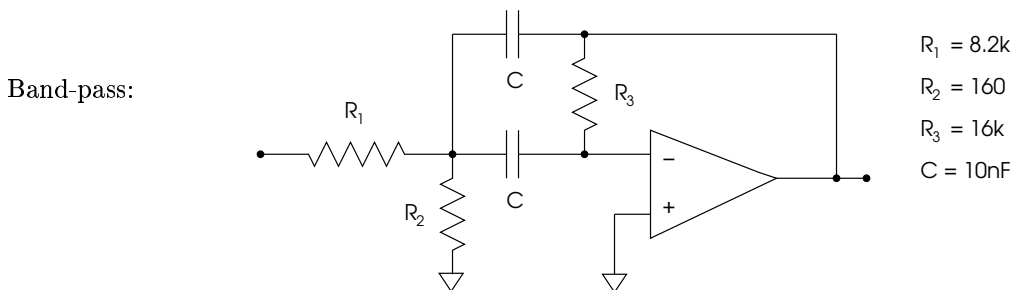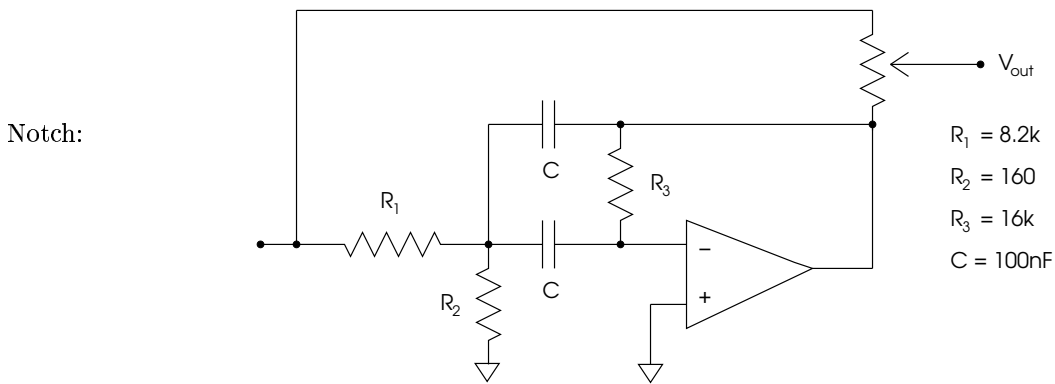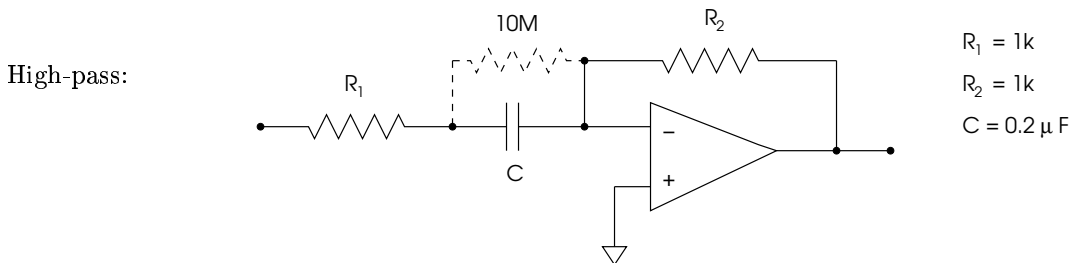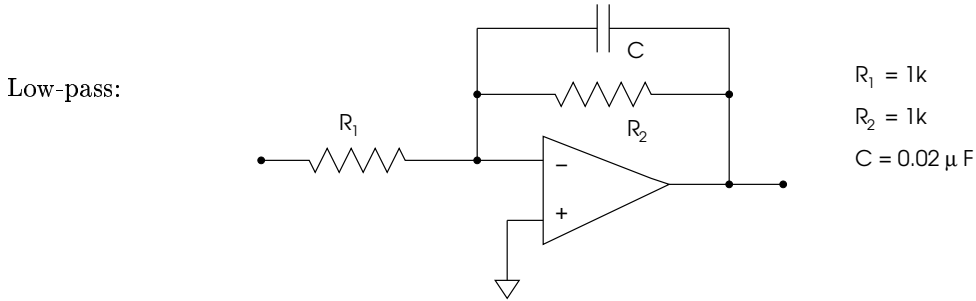2. Active Filters

- Build one of the following active filter designs. Try and build a different one from your neighbor.



- Alternatively you can look at the handout from *Horowitz and Hill* to design and build a Butterworth, Chebyshev, or Bessel filter. Use as many poles as you dare using parameters from Table 4.2.
- Using the frequency counter to monitor frequency, measure your filters transfer function, including phase.
- Plot the transfer function. You can do this after lab with a plotting program if you like, but make a rough sketch in your lab book.
- Finally, cascade your filter with another (or several to make a super filter) and observe the different response. Measure the transfer function and compare it with the individual functions.